


Module 3 : Bipolar Junction Transistors.

Diode is a two-layers, one-junction Semiconductor device which conducts current in a particular ~~operation~~ direction and whose magnitude is controlled by external circuit supply.


A transistor is a combination of two back to back diodes. It is 3 layer 2-junction device which has npn and pnp form and is called a transistor. With a terminal connected to each layer, it acts as a two port device wherein one of the terminals is common between the two ports. Such a transistor is known as Bipolar Junction Transistor (BJT) which acts as a current-controlled device with the output current being controlled by the input current.

A BJT can be used as an amplifier or a Switch.


BJT construction and operation.

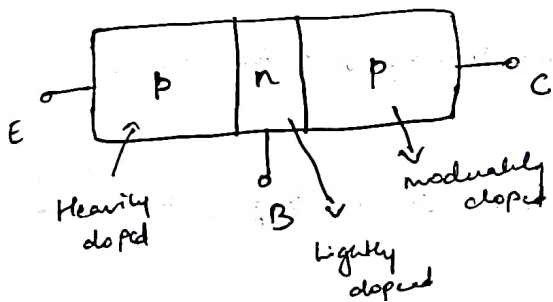


PNP transistor.

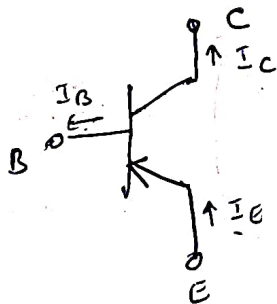

PNP transistor symbol.

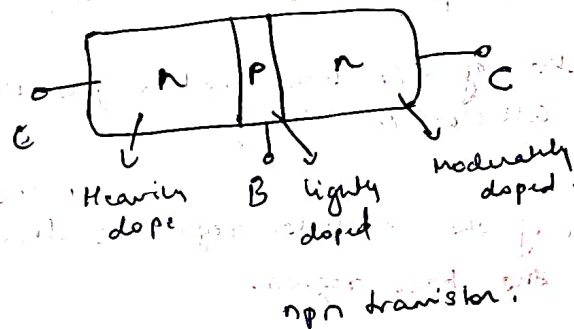

nPN transistor.

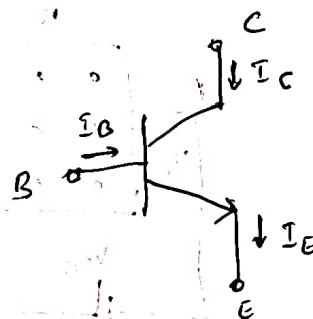


nPN transistor symbol.


There are 2 junction: EB junction and CB junction. A transistor is like 2 diodes.

EB Junction : Forward Biased diode

CB Junction : Reverse Biased diode.

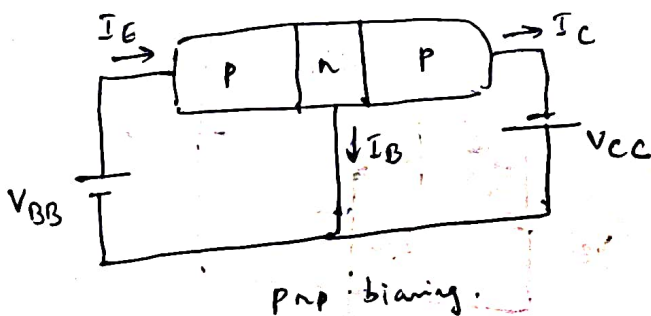


PNP biasing.

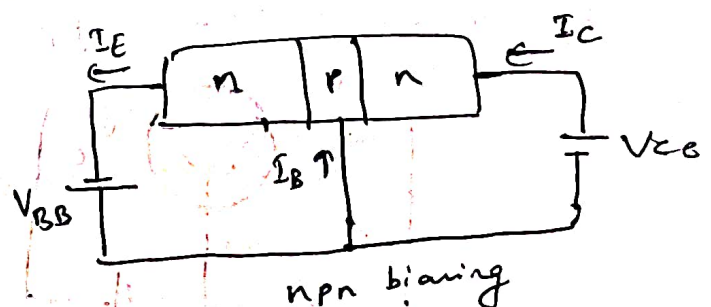

nPN biasing


- * Two pn junctions are formed with depletion regions and barrier voltage at each junction.
- * The barrier voltages are negative on the p-side and positive on the n-side.
- * EB is forward biased, so that the charge carriers are emitted into the base.
- * CB is reverse biased and its depletion region penetrates deep into base.
- * Base section is made as narrow as possible so that charge carriers move easily from emitter to collector.
- * Base is lightly doped, so that few charge carriers are available to recombine with the majority charge carriers from the emitter.
- * Most charge carriers from the emitter flow to the collector, a few flow out through the base terminal.
- * Variation of the base-emitter junction bias voltages affects the base, emitter and collector currents.
- * Width of the collector region is ~~less~~ ^{more} than the emitter region ~~but more~~ ^{and more} than the base region.

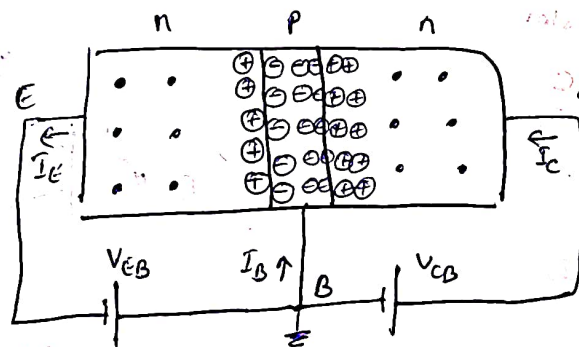


Factor affecting width of the depletion region
 (inversely proportional)
 \rightarrow Dopant Concentration
 \rightarrow Reverse bias
 \rightarrow Forward bias.

BJT Configurations:

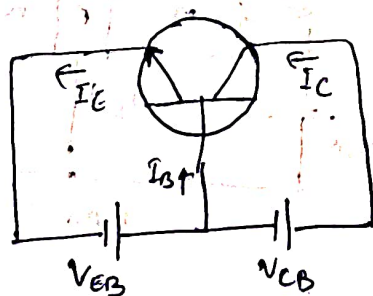1. Common Base Configuration
2. Common Emitter configuration
3. Common collector configuration.



CB configuration

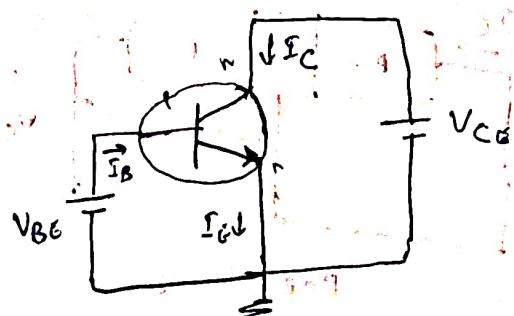

CE configuration.

BJT current components.

Emitter current relation with collector and base currents is given by

$$I_E = I_C + I_B$$

When emitter circuit is open, there is no supply of free electrons from emitter to collector. Even then, there is a small amount of collector current called reverse saturation current I_{CBO} (due to thermally generated electron-hole pairs).

Total collector current is

$$I_C = K_{dc} I_E + I_{CBO}$$

Where K_{dc} is fraction of emitter current that flows to the collector

$$\text{Common base dc current gain } K_{dc} = \frac{I_C - I_{CBO}}{I_E}$$

Since I_{CBO} is very small,

$$K_{dc} = \frac{I_C}{I_E}$$

Also
Common emitter dc current gain $B_{dc} = \frac{I_C}{I_B}$, another symbol h_{fe}

Relation b/w current gains K_{dc} and B_{dc}

$$B_{dc} = \frac{K_{dc}}{1 - K_{dc}}$$

When $I_B = 0$, $I_C = I_{CEO}$ (Collector cut off current).

$$I_{CEO} = \frac{I_{CBO}}{1 - K_{dc}}$$

Terminal Voltages.

For NPN, Base bias voltage V_B connected via Resistor R_B and collector supply V_{CC} is connected via R_C .

$$V_{CC} \gg V_B$$

Typical base emitter voltages - 0.7V for Si, 0.3V for Ge transistor.

Typical collector voltages - 3V to 20V for most transistors.

Q. Calculate I_C and I_E for a transistor that has $K_{dc} = 0.98$ and $I_B = 100 \mu A$.
Determine the value of B_{dc} (or h_{fe}) for the transistor.

$$K_{dc} = 0.98$$

$$B_{dc} = \frac{K_{dc}}{1 - K_{dc}} = \frac{0.98}{1 - 0.98}$$

$$= 49$$

$$\beta_{dc} = \frac{I_C}{I_B}$$

$$I_C = \beta_{dc} \cdot I_B$$

$$= 49 \times 100 \times 10^{-6}$$

$$= 4.9 \text{ mA}$$

$$I_E = \frac{I_C}{\alpha_{dc}} = \frac{4.9 \times 10^{-3}}{0.98}$$

$$= 5 \text{ mA}$$

Q. Calculate α_{dc} and β_{dc} for the transistor (Q1) if I_C is measured as 1 mA and I_B is 25 μA . Determine the new base current to give $I_C = 5 \text{ mA}$.

$$\beta_{dc} = \frac{I_C}{I_B}$$

$$= \frac{1 \times 10^{-3}}{25 \times 10^{-6}} = 40$$

$$I_E = I_C + I_B = 1.025 \text{ mA}$$


$$\alpha_{dc} = \frac{I_C}{I_E} = \frac{10^{-3}}{1.025 \times 10^{-3}}$$

$$= 0.976$$

New base current $I_B = \frac{I_C}{\beta_{dc}}$

$$= \frac{5 \text{ mA}}{40} = 125 \text{ } \mu\text{A}$$

BJT Characteristics: CB Characteristics.

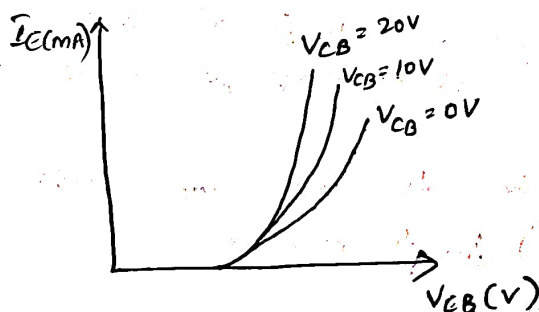


Input characteristics

(Plot of input current versus i/p voltage for const value of output voltage V_{CB} .)

As V_{EB} is increased, I_E increases. The characteristics curve is similar to diode characteristics.

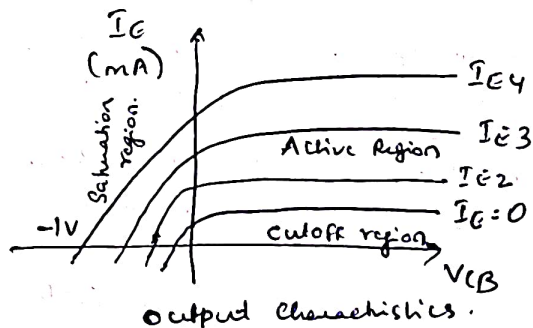If V_{CB} is increased, then I_E shoots up early. This is due to the increase in electric field aiding the flow of electrons from emitter.





Output characteristics is a plot of I_C versus output voltage V_{CB} for various const values of input current I_E . characteristics is divided into 3 regions namely Active, Saturation and cut off region.

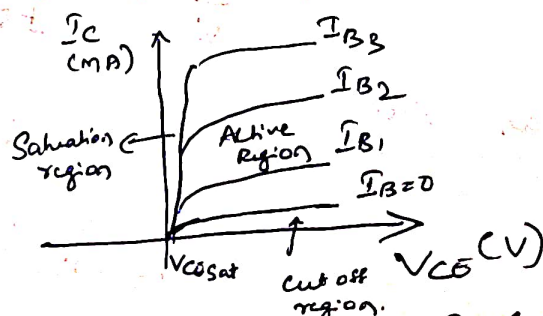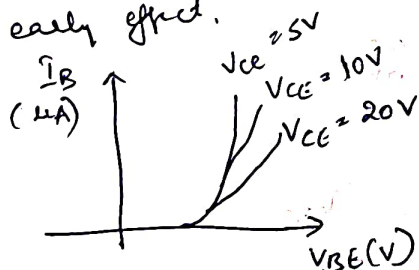- a) **Active Region** — Region to the right of y-axis above $I_E = 0$ curve. Where the curves are linear.
 I_E is positive non zero (i.e. E-B diode is forward biased) and V_{CB} is positive (C-B diode is reverse biased).
 When V_{CB} is increased I_C increases slightly. This is because, when V_{CB} is increased, depletion region width at C-B junction increases, effectively base width decreases and hence I_B decreases. Due to this collector current I_C increases. This effect is known as Early effect (modulation).
 If I_E is increased to higher const value, I_C also increases.
 When $I_E = 0$, $I_C = I_{CBO}$. I_{CBO} doubles for every ten degree rise in temperature.
- b) **Saturation Region**. This is the region to the left of y-axis above $I_E = 0$ curve. In this I_E is positive non zero (E-B diode forward biased) and V_{CB} is negative (C-B diode is forward biased), I_C decreases exponentially in this region.
- c) **Cut off region**: This is the region below $I_E = 0$ curve. In this emitter current I_E is less than zero (E-B diode is reverse biased) and collector to base voltage V_{CB} is positive (C-B diode is reverse biased). Transistor is said to be in off state since $I_C = 0$.

Common Emitter Input and output characteristics

Input characteristics of CE is a plot of input current I_B versus input voltage V_{BE} for various values of output voltage V_{CE} . As V_{BE} is increased, I_B increases. The characteristic curve is similar to diode characteristics. If V_{CE} is increased to higher const value, then I_B decreases slightly. This is due to early effect.



Active Region — Region to the right of V_{CEsat} above $I_B = 0$ curve.
 $V_{CE} = V_{CB} + V_{BE}$. If $V_{CE} > V_{CESat}$, then V_{CB} becomes positive (C-B diode is reverse biased). If $V_{BE} > 0$, E-B is forward biased.



Saturation region - Region to the left of V_{CEsat} and right of y-axis.

Region E-B diode and C-B diode are both forward biased.

Cut off region - Region below $I_B = 0$ curve. In this E-B diode and C-B diode are both reverse biased. Transistor is said to be in OFF state. Since I_C is almost zero.

BJT as an amplifier.

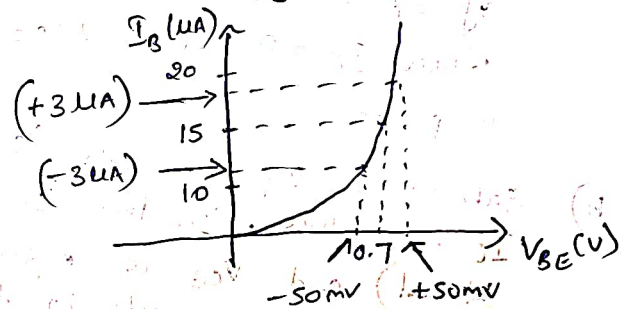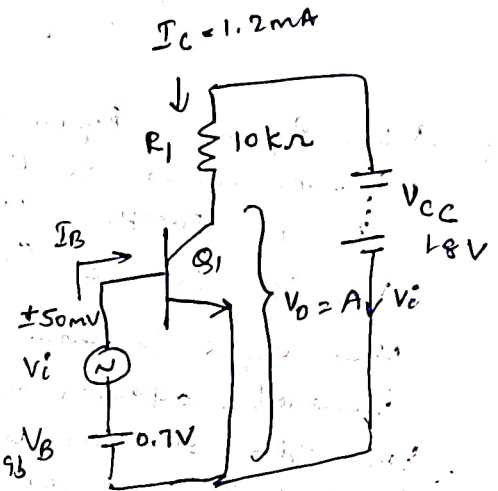Determine the dc collector voltage for the circuit in Fig. 4-19a if the transistor has I_B/V_{BE} characteristics shown in Fig. 4-19b and $\beta_{dc} = \beta_{ac} = 80$. Calculate the circuit voltage gain when $V_i = \pm 50mV$.



$$I_B = 15 \mu A, V_B = 0.7V$$

$$I_C = \beta_{dc} I_B = 80 \times 15 \mu A = 1.2mA$$

$$V_C = V_{CC} - (I_C R_1) = 18 - (1.2mA \times 10k\Omega) = 6V$$


$$I_B = \pm 3 \mu A \text{ for } V_i = \pm 50mV$$

$$I_C = \beta_{ac} I_B = 80 \times \pm 3 \mu A = \pm 240 \mu A$$


$$I_C \cdot R_1 = \pm 240 \mu A \times 10k\Omega = \pm 2.4V$$

$$A_v = \frac{V_o}{V_i} = \frac{\pm 2.4V}{\pm 50mV} = 48$$

BJT as switch.

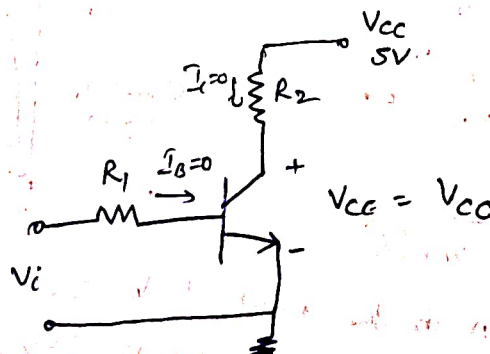

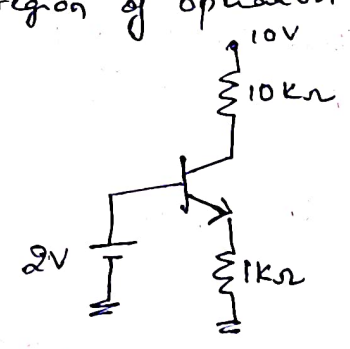Q. Find the region of operation, if β is very large & $V_{BE} = 0.7V$



$\beta \gg \text{large}$, I_B very small,
 $\Rightarrow I_E \approx I_C$

B-E junction is forward biased since p - +ve terminal, n to -ve terminal.

$$10 = 10 \times 10^3 \times I_C + V_{CB} + 2$$

$$8 = 10 \times 10^3 \times I_C + V_{CB}$$

$$2 = V_{BE} + I_E \times 10^3$$

$$= V_{BE} + (I_C + I_B) \times 10^3$$

$$1.3 = \frac{\beta}{\beta + 1} I_C \times 10^3$$

$$I_C = 1.3 \text{ mA}$$

$$8 = 10 \times 10^3 \times 1.3 \times 10^{-3} + V_{CB}$$

$$V_{CB} = -5V$$

$V_{CB} \rightarrow -ve \Rightarrow V_{CB} \rightarrow \text{forward biased.}$


$V_{CE} = V_{CB} = -5$ Transistor is in saturation region.

Q. Find the region of operation if $\beta = 100$, $V_{CEsat} = 0.2V$, $V_{BEsat} = 0.8V$

$$5 = 50 \times 10^3 I_B + 0.8$$

$$I_B = \frac{4.2}{50 \times 10^3}$$

$$= 0.084 \text{ mA}$$

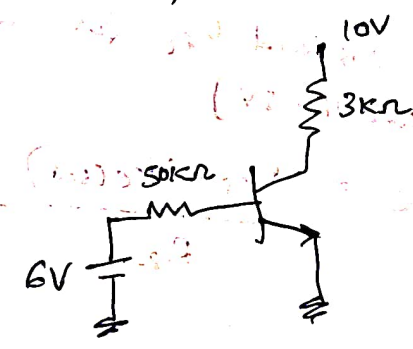

$$10 = 3 \times 10^3 I_C + V_{CEsat}$$

$$9.8 = 3 \times 10^3 I_C$$

$$I_C = \frac{9.8}{3 \times 10^3} = 3.267 \text{ mA} = I_{C(sat)}$$

$$I_{Bmin} = \frac{I_{C(sat)}}{\beta} = \frac{3.267 \times 10^{-3}}{100} = 0.0327 \text{ mA}$$

$$10 = 3 \times I_C + V_{CE} + 50 \times I_B + 6$$

$$4 = 9.801 + V_{CB} + 4.2$$

$$V_{CB} = -10V$$

Since $I_B > I_{Bmin}$, transistor is in saturation region.


BJT as a switch.

The switching circuit is similar to an amplifier circuit except that a pulse waveform input, instead of a bias voltage and ac signal source is applied to the transistor base.

When the input voltage V_i is at zero level, the base current I_B is zero and consequently I_C is zero.

$$V_{CE} = V_{CC} - I_C R_2$$
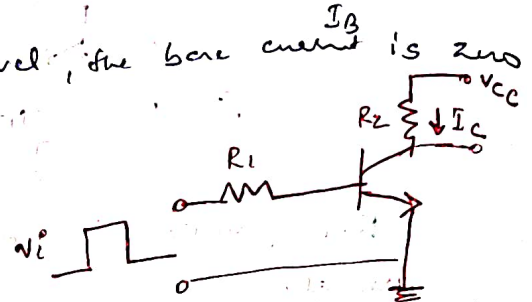
$$\text{With } I_C = 0 \quad V_{CE} = V_{CC}$$



When V_i is at a +ve level, a base current flows. In a switching circuit I_B is made large enough to produce an I_C level that will cause the voltage drop across R_2 to approximately equal the supply voltage.

$$V_{CE} \approx V_{CC} - I_C R_2 \quad (I_C R_2 \approx V_{CC})$$
$$\approx 0$$

If V_{CE} went down to exactly zero volts, the C-B junction would become forward biased by 0.7V. In this case, collector base barrier voltage would be overcome and charge carriers from the emitter would be repelled from the collector-base junction. Consequently there would be zero collector current. But if I_C becomes zero, there would be no voltage drop across R_2 and the collector-emitter junction would not be forward biased. So I_C does flow, but it does not become large enough to make V_{CE} equal zero.

Q Calculate I_C , I_B and h_{FE} for switching circuit when Q_1 is switched into saturation. [Take $V_i = 2V$]

$$I_C = \frac{V_{CC} - V_{CE(sat)}}{R_2} = \frac{5 - 0.2}{4.7k\Omega}$$
$$= 1.02 \text{ mA}$$

$$I_B = \frac{V_i - V_{BE}}{R_1} = \frac{2 - 0.7}{12k\Omega} = 108 \mu\text{A}$$

$$h_{FE} = \frac{I_C}{I_B} = 9.4$$

Determine R_B and R_C for a transistor circuit shown in fig. $I_{C(sat)} = 5\text{mA}$ and $V_{CE(sat)} = 0.2\text{V}$, $V = 5\text{V}$


$$R_C = \frac{V_{CC} - V_{CE(sat)}}{I_{C(sat)}}$$

$$= \frac{12 - 0.2}{5 \times 10^{-3}} = 2.7\text{k}\Omega$$

$$I_{B(min)} = \frac{I_C}{\beta_{dc}} = \frac{5 \times 10^{-3}}{200} = 25\mu\text{A}$$

$$R_B = \frac{V_B - V_{BE}}{I_{B(min)}}$$
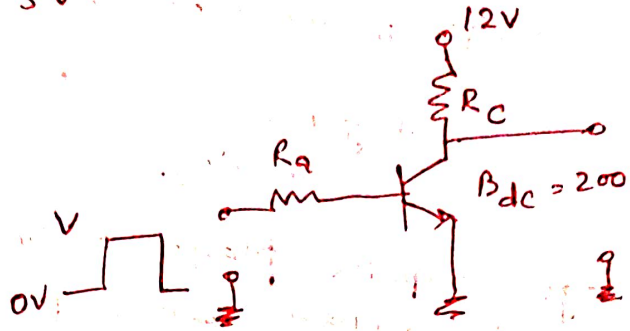
$$= \frac{5 - 0.7}{25 \times 10^{-6}} = 172\text{k}\Omega$$



$I_B > I_{B(min)}$
for
saturation
region.