

## Module - 1

### Semiconductor Diodes

Diodes

+

Rectifiers.




Dr. Sumal Unmesh  
EEE Dept.  
BMSIT&M.

## Semiconductor Diodes

- \* The term diode refers to a two-electrode or two-terminal semiconductor device.
- \* It is a pn-junction with a connecting lead on each side.
- \* A diode is a one-way device : offers low resistance to current flow when forward-biased and offers high resistance and acts as open switch when reverse-biased.
- \* A constant voltage drop occurs across a forward biased diode.


## Pn junction Diode

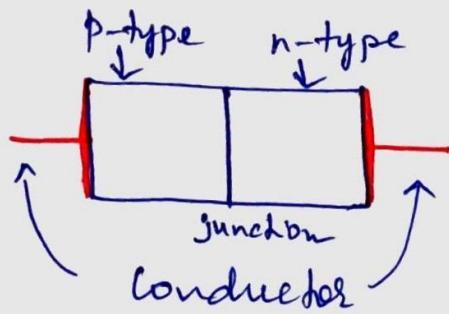

A pn junction permits substantial current flow when forward-biased, and blocks current when reverse-biased. Thus, it can be used as a switch: It's ON when forward biased and OFF when reverse biased.

A pn junction provided with copper wire connecting leads becomes an electronic device known as diode.

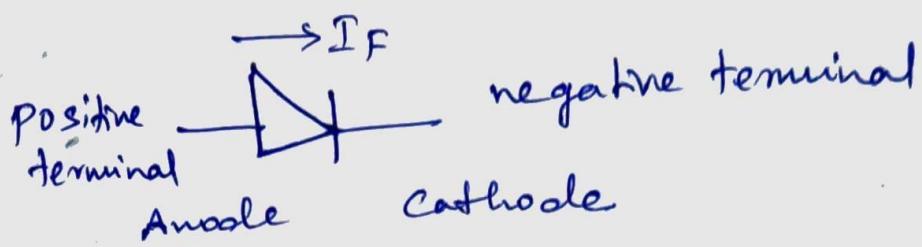The circuit symbol for a diode is as shown below.



The arrow head indicates the conventional direction of current flow. When diode is forward biased.

The p-side is always the positive terminal and is termed as Anode.

The n-side is always the negative terminal and is termed as cathode.


- A pn junction diode can be destroyed
- when a high magnitude of forward current overheats the device
  - or a large reverse voltage causes the junction to breakdown.

For this reason, the maximum forward current & maximum reverse voltage for diodes are specified on the manufacturer's data sheet.
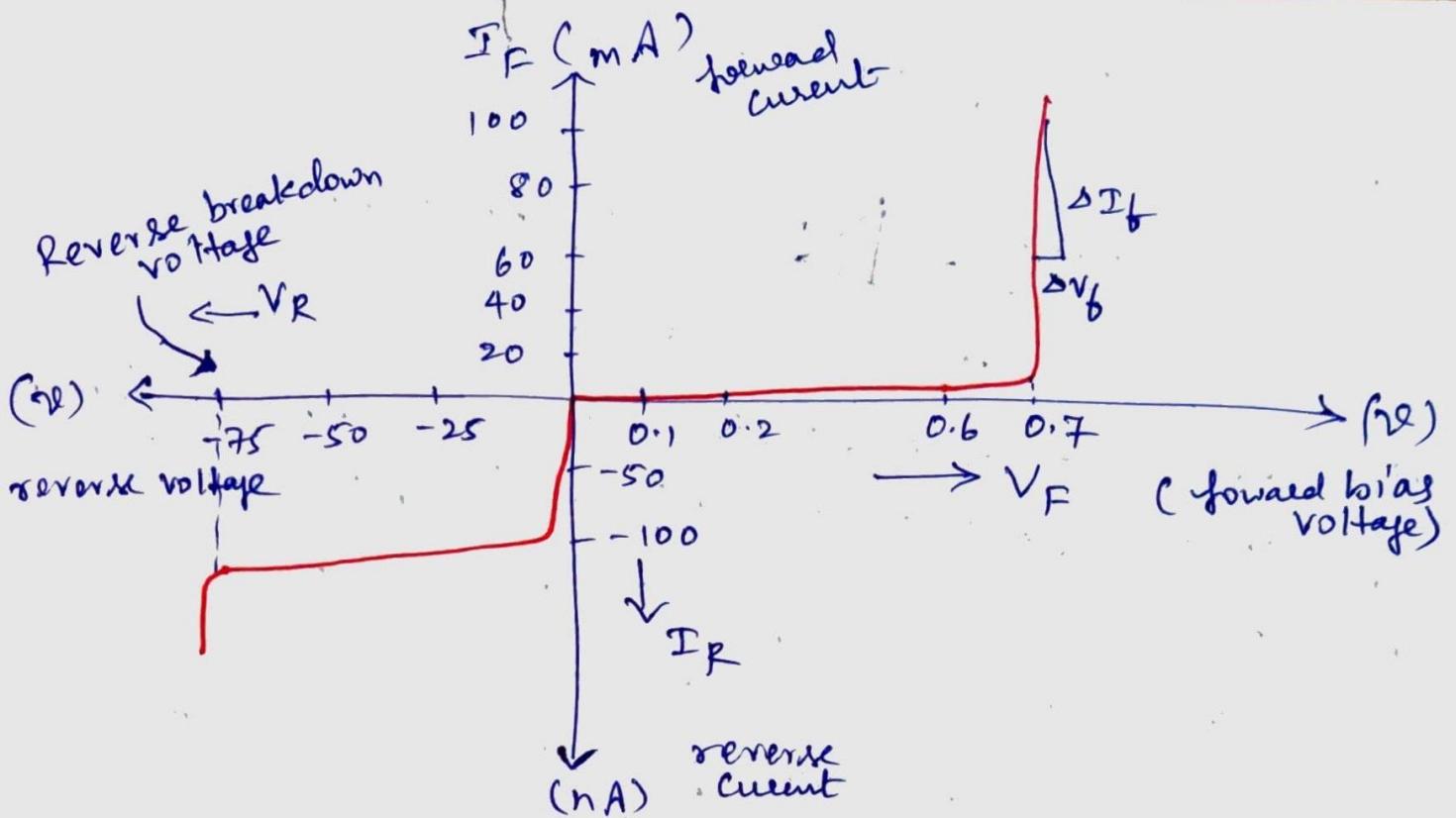
### Characteristics and Parameters of a Diode

There are two characteristics for a diode namely:

- ① Forward characteristics
- ② Reverse characteristics.



Typical forward & Reverse characteristics of a silicon diode.

From the above diagram, which depicts the forward characteristics (1<sup>st</sup> quadrant) and reverse characteristics (3<sup>rd</sup> quadrant) for a silicon diode, it is clear that

- \* The forward current ( $I_F$ ) remains very low until the diode forward bias voltage ( $V_F$ ) exceeds approximately 0.7 V. After  $V_F$  becomes greater than 0.7 V,  $I_F$  increases linearly.

- \* The reverse current ( $I_R$ ) is very much smaller than its forward current. (Therefore, the scale of reverse characteristics is in nA) The  $I_R$  is normally less than 100 nA. and is almost completely independent of

of reverse-bias voltage. The reverse

- \* The reverse current is usually less than  $\frac{1}{10,000}$  of the lowest normal forward current.  
Therefore the reverse-biased diode may be treated almost as an open switch.
- \* When diode reverse voltage ( $V_R$ ) is sufficiently increased, the device goes into reverse breakdown.  
For silicon, this occurs at  $V = -75V$ .

### Diode Parameters:

The important diode parameters are:

- (i) Forward voltage drop ( $V_F$ )
- (ii) Reverse saturation current ( $I_R$ )
- (iii) Reverse breakdown voltage ( $V_{BR}$ )
- (iv) Dynamic resistance ( $r_d$ )
- (v) Maximum forward current,  $I_{F(\max)}$

Normally these parameters are listed on the diode data sheet provided by the device manufacturer.

Forward voltage drop  $V_F$  for silicon is approximately  $V_F \approx 0.7V$ .

It is the voltage across the diode when it is conducting (ON)

Reverse saturation current ( $I_R$ ) is the leakage current when diode is not conducting (OFF)  
for silicon it is  $I_R \approx 100nA$ .

Reverse breakdown voltage: It is the reverse voltage value at which the pn junction breaks down and reverse current increases drastically, and damages the diode.

for silicon  $V_{BR} = 75V$ .

The dynamic resistance of the diode is the resistance offered to changing levels of forward voltage. It is given by the formula

$$r_d = \frac{\Delta V_F}{\Delta I_F}$$

(This can be calculated from the slope of the forward characteristics)


It is also calculated by the rule-of-thumb equation

$$r_d' = \frac{26mV}{I_F}$$

Thus for example, if for a diode passing a 1mA forward current,

$$r_d' = \frac{26mA}{1mA} = \underline{\underline{26\Omega}}$$

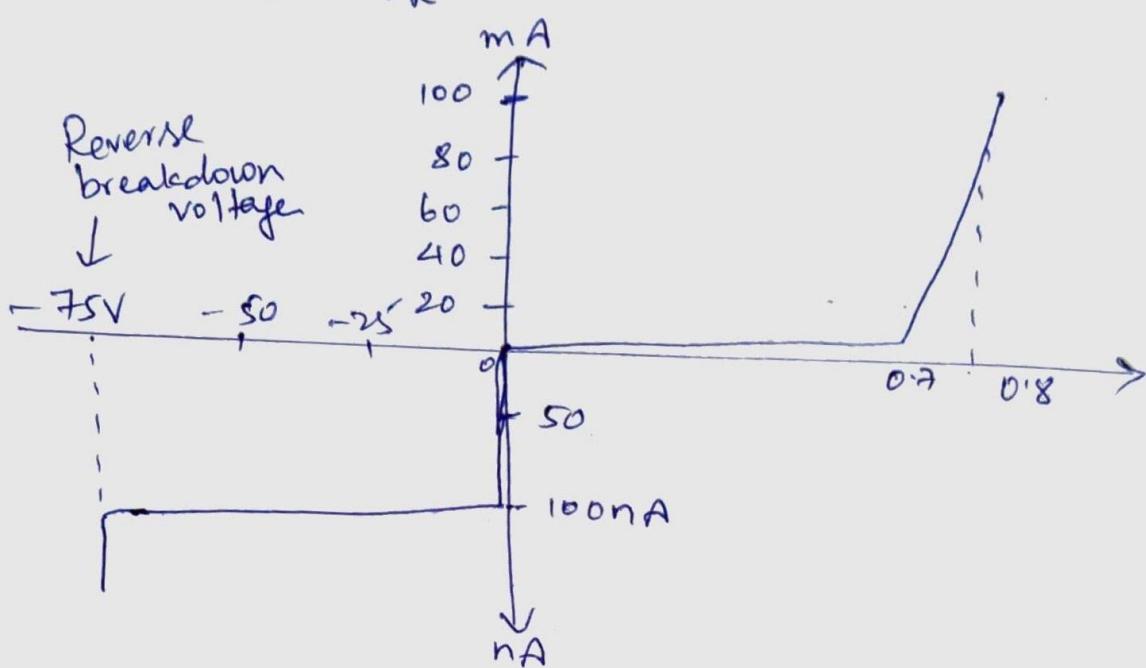1) Calculate the forward and reverse resistance offered by a silicon diode with the characteristics as in the below figure at  $I_F = 100\text{mA}$  and at  $V_R = 50\text{V}$ .



From the characteristics,

$$\text{At } I_F = 100\text{mA}, V_F = 0.75\text{V}.$$

The Forward resistance ( $R_F$ ) of a diode is represented as

$$\downarrow \quad \begin{array}{c} + \\ \text{---} \\ \text{---} \end{array} \quad \left. \begin{array}{l} + \\ - \end{array} \right\} V_F \quad \left. \begin{array}{l} + \\ - \end{array} \right\} R_F = \frac{V_F}{I_F}$$

$$\therefore R_F = \frac{V_F}{I_F} = \frac{0.75}{100 \times 10^{-3}} = \underline{\underline{7.5\Omega}}$$

The reverse resistance ( $R_R$ ) of a diode is represented as


$$\downarrow \quad \begin{array}{c} + \\ \text{---} \\ \text{---} \end{array} \quad \left. \begin{array}{l} + \\ - \end{array} \right\} V_R \quad \left. \begin{array}{l} + \\ - \end{array} \right\} R_R = \frac{V_R}{I_R}$$

From the characteristics,  $V_R = 50\text{V}$ ,  $I_R = 100\text{nA}$

$$\therefore R_R = \frac{V_R}{I_R} = \frac{50}{100 \times 10^{-9}} = \underline{\underline{500\text{M}\Omega}}$$

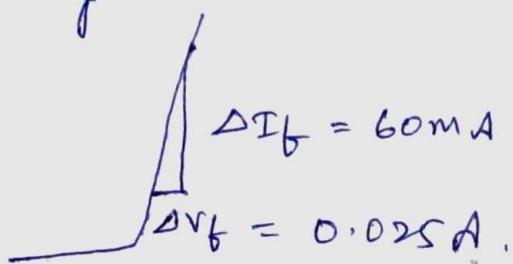- 2) Determine the dynamic resistance at a forward current of 70mA for the diode characteristic given

The dynamic resistance ( $r_d$ ) of a diode is given by



$$r_d = \frac{\Delta V_f}{\Delta I_f}$$


from characteristics, at  $I_F = 70\text{mA}$ ,

$$\Delta I_f = 60\text{mA} \quad \cancel{\Delta I_f = 60\text{mA}}$$

$$\Delta V_f \approx 0.025\text{V}.$$

$$r_d = \frac{\Delta V_f}{\Delta I_f} = \frac{0.025}{60\text{m}} \\ = \underline{\underline{0.425}}$$

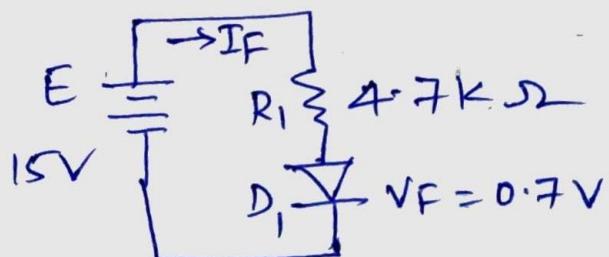- ③ A silicon diode is used in the cbt shown calculate diode current.



Soh: The circuit forms a closed loop with a series current  $I_F$  in the loop.

APPLY KVL to the loop:

$$E = IFR_1 + V_F$$

For a forward biased diode  $V_F = 0.7V$ .

$$\therefore IFR_1 = E - V_F$$

$$I_F = \frac{E - V_F}{R_1}$$

$$= \frac{15 - 0.7}{4.7 \times 10^3}$$

$$I_F = \underline{\underline{3.04mA}}$$


## Diode Applications

One of the most important applications of diodes is rectification; which is conversion of a sinusoidal ac waveform into single-polarity half cycles.

Rectification may be performed by half-wave or full-wave rectifier circuits.
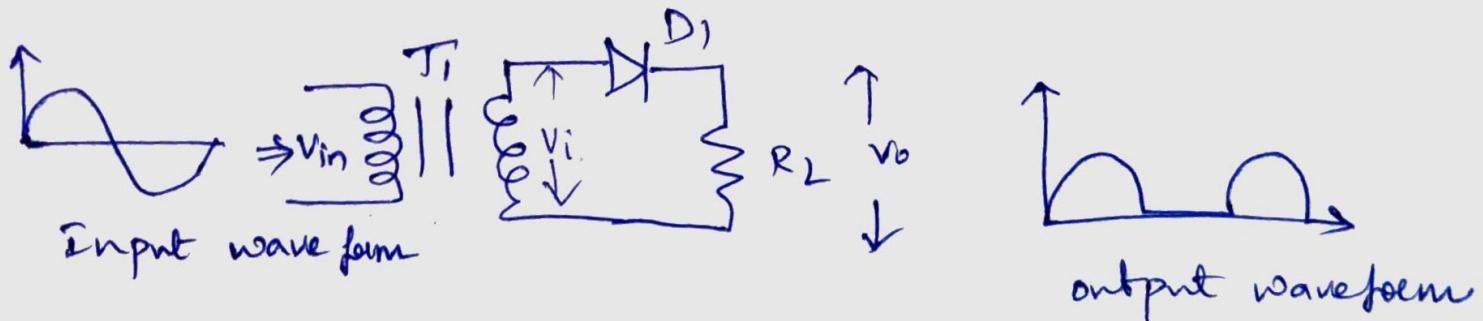
### (a) Half-Wave Rectification

A diode half wave rectification circuit is shown in the figure below:




$T$  = transformer

$D_1$  = diode    &  $R_L$  = output/load resistance

An alternating input voltage is applied via transformer ( $T_1$ ) to a single diode ( $D_1$ ) connected in series with a load resistor  $R_L$ . The transformer steps down the higher input voltage to a lower magnitude as well as it isolates the dc-side of the rectifier from the ac-supply.

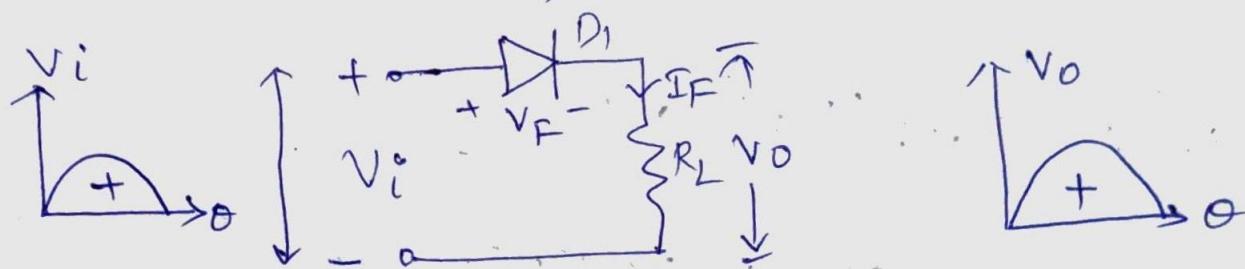During the positive half cycle, the diode is forward biased, as shown below.



The voltage drop across the diode during positive half cycle is  $V_F$ . The output voltage across  $R_L$  which is  $V_O$  is  $V_i - V_F$ .

Therefore the peak output voltage is given by

$$V_{po} = V_{pi} - V_F$$

where  $V_{pi}$  = peak input voltage =  $\sqrt{2} V_{(RMS)}$ ;

The diode peak forward current is given by

$$I_p = \frac{V_{po}}{R_L}$$


During the negative half cycle, the diode is reverse biased and offers very high resistance to current. Therefore, there is only a <sup>very</sup> small reverse current flowing.

The output voltage

$$-V_o = -I_R R_L$$

Since the current  $I_R$  is very small, practically  $V_o$  is zero.

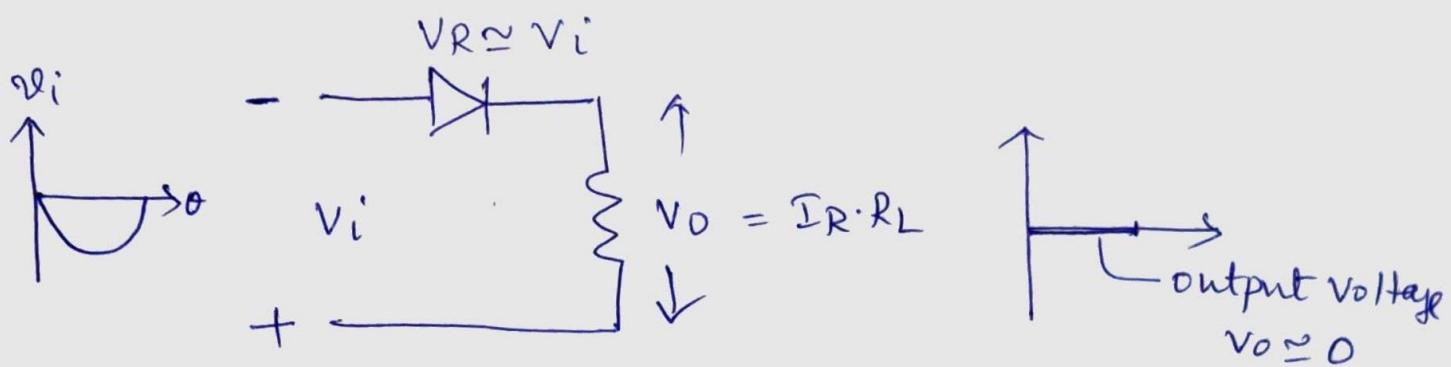
Hence after the diode reverse bias, the peak voltage of negative half cycle of the input appears fully across the diode.



The peak reverse voltage or peak-inverse voltage (PIV) is given by

$$V_R = PIV = V_{pi}$$

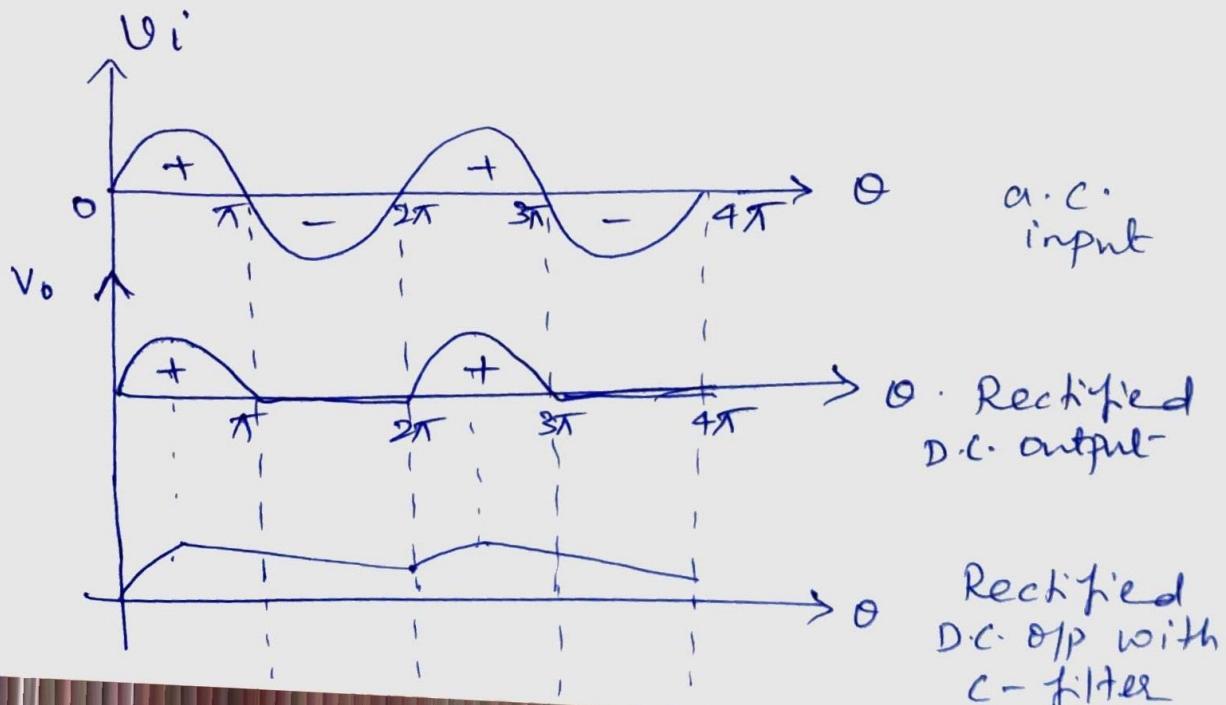Thus for one full cycle of input a.c. voltage the output voltage is represented as



The average and RMS value of rectified D.C. output voltage is given by the formula : The pulsating DC O/P has both a.c. + d.c. component.

D.C. component

$$V_o(\text{avg}) = \frac{V_{po}}{\pi} = 0.318 V_{po}$$

a.c. component

$$V_o(\text{RMS}) = \frac{V_{po}}{2} = 0.5 V_{po}$$

- ) A diode with  $V_F = 0.7\text{V}$  is connected as a half-wave. The load resistance is  $500\Omega$ . The rms input a.c. is  $22\text{V}$ . Determine the peak output voltage, peak load current and diode peak reverse voltage.

Soh. The peak input voltage

$$\begin{aligned} V_{pi} &= \sqrt{2} V_i = 1.414 \times 22 \\ &= \underline{\underline{31.1\text{V}}} \end{aligned}$$


$$\begin{aligned} V_{po} &= V_{pi} - V_F \\ &= 31.1 - 0.7 \\ &= \underline{\underline{30.4\text{V}}} \end{aligned}$$

$$I_p = \frac{V_{po}}{R_L} = \frac{30.4}{500} = \underline{\underline{60.8\text{mA}}}$$

$$PIV = V_{pi} = \underline{\underline{31.1\text{V}}}$$

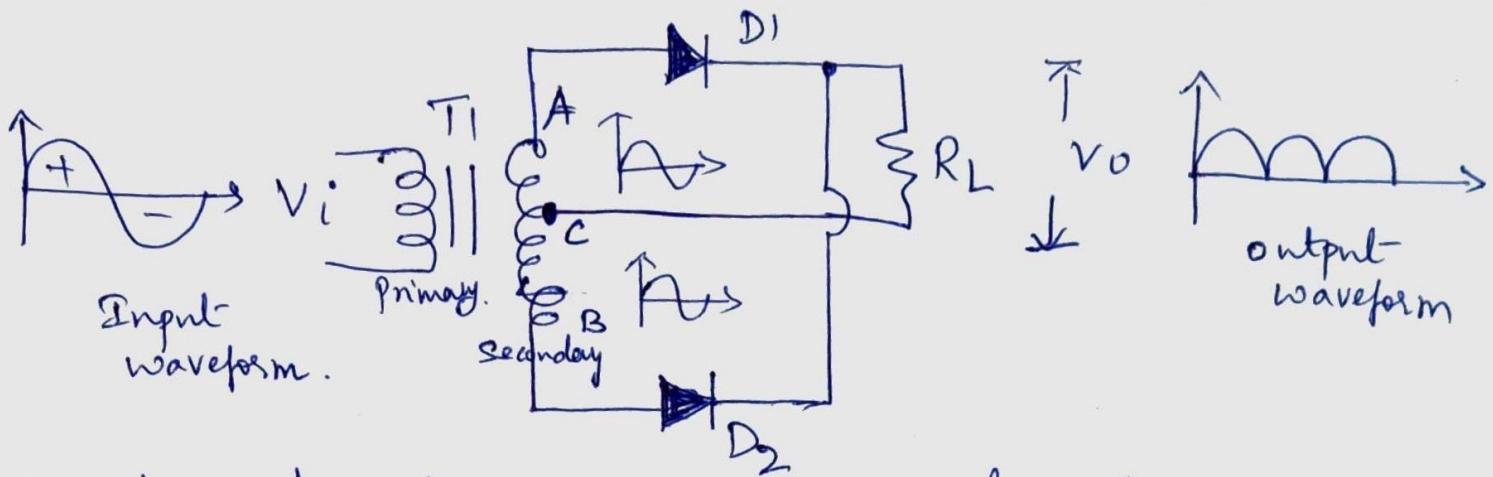(b) Full-Wave Rectification:

The full-wave rectifier uses two diodes and input is supplied from a transformer (T1). The circuit is essentially a combination of two half wave rectifier circuits, each supplied from one half of the transformer Secondary.



on the transformer secondary side, there are 3 ends : top end - A.

bottom end - B

centre tap - C.


When top end A is positive, during positive half cycle of input, D1 is forward biased. The current flows from D1 via  $R_L$  back to centre tap point C. of the transformer.

During this positive half cycle, the bottom end point is negative and D2 is reverse biased.



When bottom end B is positive, during negative half cycle of the input, D2 is forward biased and current flows from bottom terminal of transformer Secondary (B) through (via) D2 and  $R_L$  from top of the secondary & back to transformer Centre-tap.

The output waveform is the combination of two half-cycles making a continuous series of positive half cycles of sinusoidal waveforms leading to full-wave rectification.

### Positive half cycle

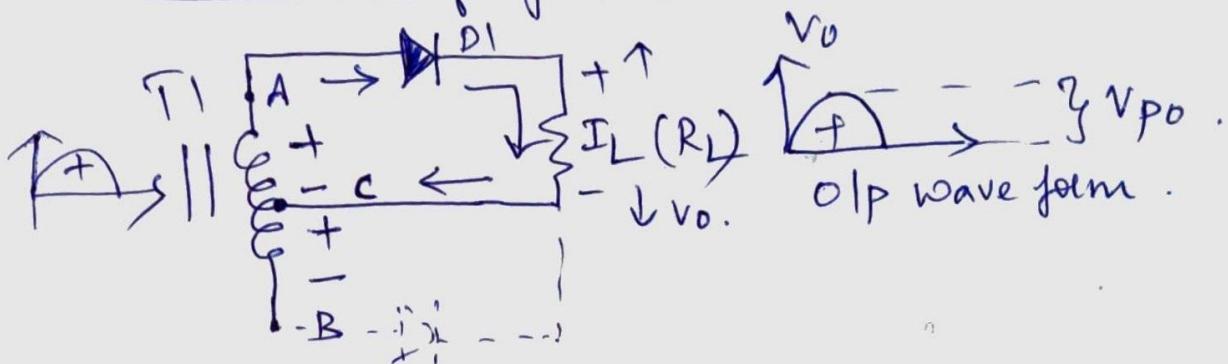

### Negative half cycle

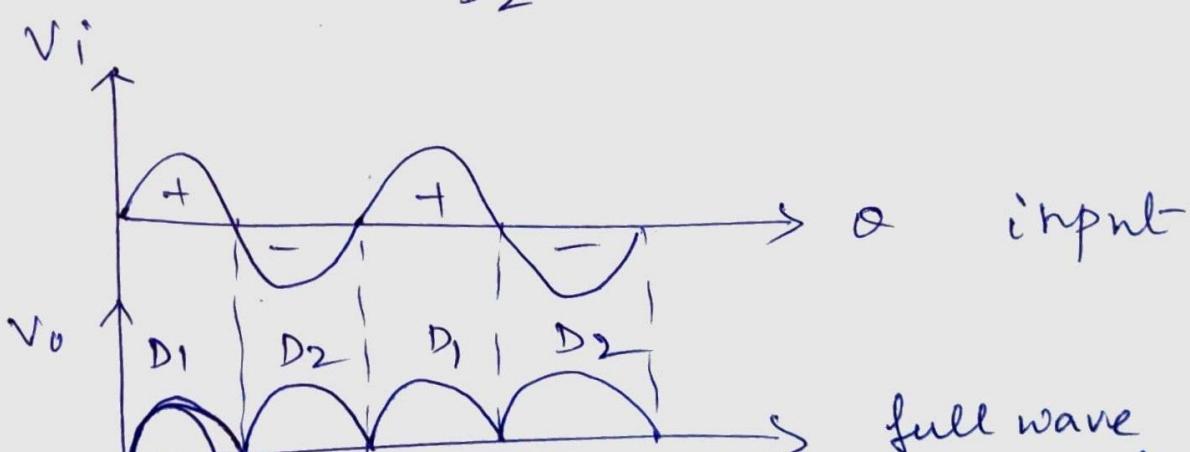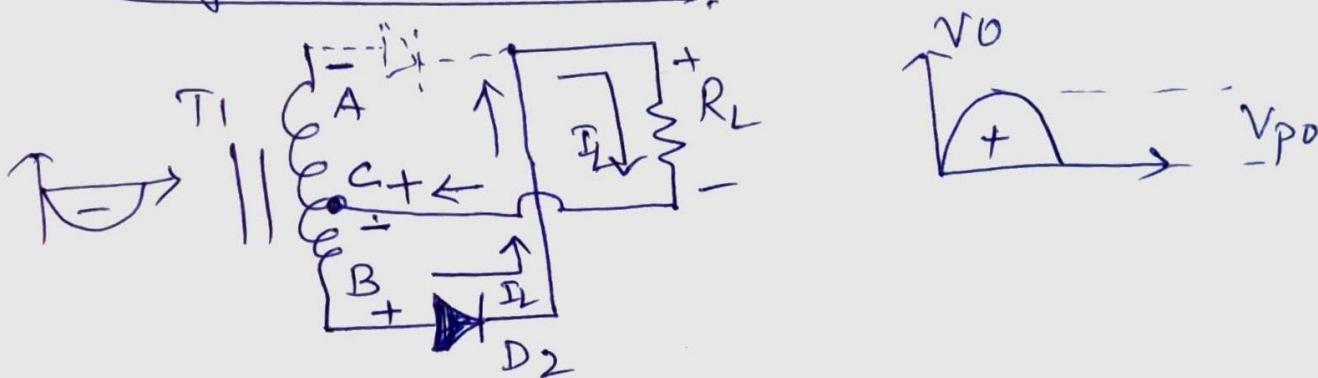


The current direction in both half cycles is same in  $R_L$ .

## Bridge Rectifier

The centre-tapped transformer used in the fullwave rectifier is usually more expensive and requires more space than additional diodes.

Therefore a bridge rectifier with 4 diodes known as bridge rectifier / full wave rectifier is most frequently used for rectification.

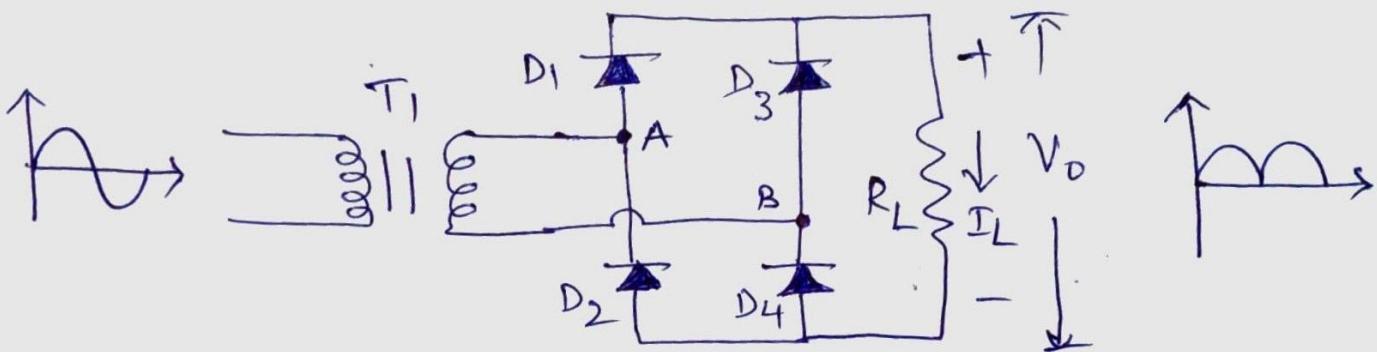The bridge rectifier consists of four diodes connected as shown below:






During the positive half cycle of input voltage, diodes  $D_1$  and  $D_4$  will conduct with terminal A being +ve and B being -ve. Load current ( $I_L$ ) flows +ve terminal A through  $D_1$  to  $R_L$  and then from  $R_L$  through  $D_4$  back to negative terminal B.

During the negative half cycle, A is -ve and terminal B is +ve therefore  $D_2$  and  $D_3$  are forward biased. The current flows from terminal B through  $D_3$  to  $R_L$  & then from  $R_L$  to negative terminal A via  $D_2$ .




Direction of current in  $R_L$  remains unchanged.

+ve half cycle.:

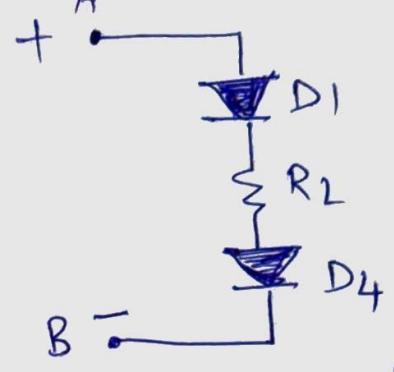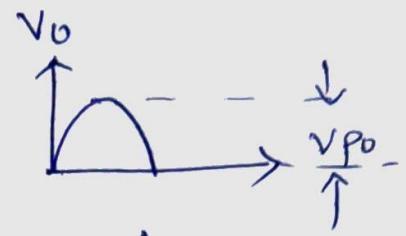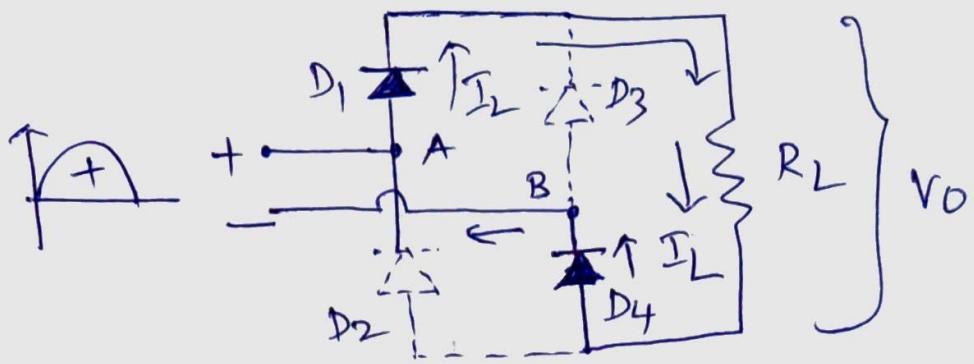

D<sub>1</sub> & D<sub>4</sub> Forward biased.

-ve half cycle.:

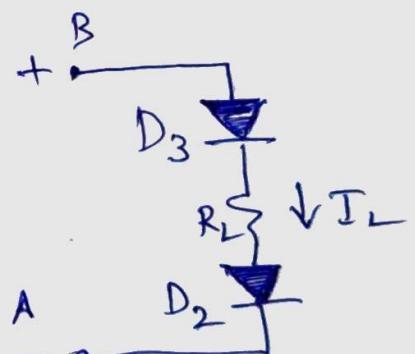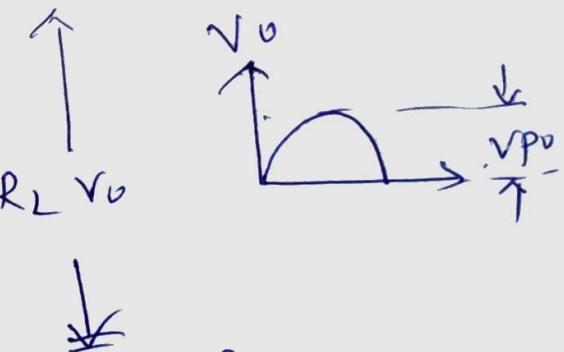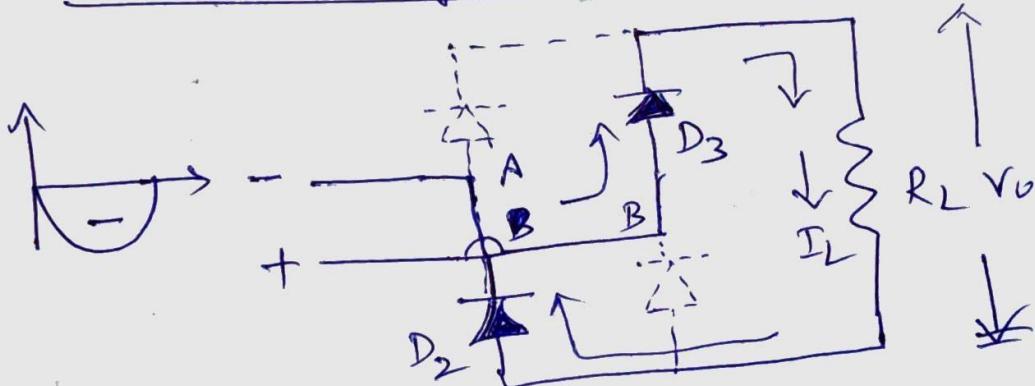

D<sub>3</sub> & D<sub>2</sub> forward biased.

The bridge rectifier has two diodes in series with the supply voltage and load. Each diode has a positive / forward voltage drop of  $V_F$ .

∴ The peak output voltage is

$$V_{PO} = V_{pi} - 2V_F$$

The output voltage will have both D.C. and A.C. component in the form of half cycles.

The average value of full-wave rectified waveform

$$V_o(\text{avg}) = 0.637 V_{po} \quad \text{D.C. component}$$

The RMS value of the full-wave rectified waveform

$$V_o(\text{RMS}) = 0.707 V_{po} \quad \text{A.C. component}$$

Ex: Determine the peak output voltage and current for the bridge rectifier when  $V_i = 30V$ ,  $R_L = 300\Omega$  and diodes have  $V_F = 0.7V$ .

Soh: the diodes input RMS  $V = 30V$

$\therefore$  Peak input voltage

$$\begin{aligned} V_{pi} &= \sqrt{2} V_i(\text{RMS}) \\ &= 1.414 \times 30 \\ &= 42.42V \end{aligned}$$

Wkt

$$\begin{aligned} V_{po} &= V_{pi} - 2V_F \quad (\text{2 diodes}) \\ &= 42.42 - (2 \times 0.7) \\ &= \underline{\underline{41V}} \end{aligned}$$

$$I_p = \frac{V_{po}}{R_L} = \frac{41}{300} = \underline{\underline{137mA}}$$